

**Broadcom**  
**BCM5208KPF**  
**Quad-PHY Transceiver**  
**Partial Circuit Analysis**  
**— Analog Circuitry —**

**Table of Contents**

<a href="#">List of Figures .....</a>	<a href="#">Page 1</a>
<a href="#">Introduction.....</a>	<a href="#">Page 3</a>
<a href="#">PLL.....</a>	<a href="#">Tab 1</a>
<a href="#">Sample and Hold.....</a>	<a href="#">Tab 2</a>
<a href="#">A/D Converter.....</a>	<a href="#">Tab 3</a>
<a href="#">D/A Converter.....</a>	<a href="#">Tab 4</a>
<a href="#">Link Detection .....</a>	<a href="#">Tab 5</a>
<a href="#">Bias Generator .....</a>	<a href="#">Tab 6</a>
<a href="#">Signal Cross-Reference .....</a>	<a href="#">Tab 7</a>

For questions, comments, or more information about this report, or for any additional technical needs concerning semiconductor technology, please call Abdullah Rahal at Chipworks.

## List of Figures

- 0.1.1 Package Markings
- 0.1.2 Package X-Ray
- 0.1.3 Pin Configuration — *(not available)*
- 0.1.4 Die Markings
- 0.2.0 Annotated Die Photograph

### **1.0.0 PLL**

- 1.0.1 DFF1 Definition
- 1.0.2 DFF2 Definition
- 1.1.0 PF Detector
- 1.2.0 Charge Pump/Loop Filter
- 1.3.0 VCO
- 1.3.1 Delay Cell
- 1.3.2 VCO Bias
- 1.4.0 Comparators
- 1.4.1 Comparator Cell
- 1.5.0 Clock Drivers
- 1.6.0 Divider
- 1.7.0 Counter

### **2.0.0 Sample and Hold**

- 2.1.0 S/H Reference
- 2.2.0 S/H circuit
- 2.2.1 S/H Amplifier
- 2.3.0 Bias Generator

### **3.0.0 A/D Converter**

- 3.1.0 Reference Generator/Pre-Amplifier
- 3.1.1 Preamp A
- 3.1.2 Preamp B
- 3.2.0 Comparators
- 3.2.1 Comparator
- 3.3.0 Decoders
- 3.4.0 Decoders

### **4.0.0 D/A Converter**

- 4.0.1 Delay Definition
- 4.0.2 MUX21 Definition
- 4.0.3 MUX81 Definition
- 4.1.0 Reference Generator
- 4.1.1 Reference Source
- 4.2.0 Current Source

- 4.3.0 Data Driver A
- 4.3.1 Data Driver B
- 4.3.2 Data Driver C

**5.0.0 Link Detection**

- 5.1.0 Input Voltage Selection
- 5.1.1 8 to 1 Multiplexer Definition
- 5.2.0 Quantizer
- 5.2.1 Amplifier Definition
- 5.2.2 Bias Voltage Generator
- 5.2.3 Sense Amplifier Definition
- 5.2.4 Clock Generator
- 5.2.5 Decision Circuit Definition
- 5.3.0 Decoder

**6.1.0 Bandgap Voltage Reference**

- 6.2.0 Bias Voltage Generator 1
- 6.3.0 Bias Voltage Generator 2
- 6.4.0 Current Sources 1
- 6.5.0 Current Sources 2
- 6.6.0 VREF Output and ESD Protection
- 6.7.0 Output Driver

---

## About Chipworks

Chipworks is the recognized leader in reverse engineering and patent infringement analysis of semiconductors and electronic systems. The company's ability to analyze the circuitry and physical composition of these systems makes them a key partner in the success of the world's largest semiconductor and microelectronics companies. Intellectual property groups and their legal counsel trust Chipworks for success in patent licensing and litigation – earning hundreds of millions of dollars in patent licenses, and saving as much in royalty payments. Research & Development and Product Management rely on Chipworks for success in new product design and launch, saving hundreds of millions of dollars in design, and earning even more through superior product design and faster launches.



## Contact Chipworks

To find out more information on this report, or any other reports in our library, please contact Chipworks at:

### Chipworks

3685 Richmond Rd.

Suite 500

Ottawa, Ontario

K2H 5B7 Canada

T: 1.613.829.0414

F: 1.613.829.0515

Web site: [www.chipworks.com](http://www.chipworks.com)

Email: [info@chipworks.com](mailto:info@chipworks.com)

Please send any feedback to  
[feedback@chipworks.com](mailto:feedback@chipworks.com)



[www.chipworks.com](http://www.chipworks.com)